

Instruction Set Architecture Embedded Systems

VeSPA

João Araújo – PG53922
Tiago Sousa – PG54261

Agenda

- Instruction Set
- Instruction Format
- Branch Conditions
- Datapath Design
- State Machine
- Test Benches
- RTL Schematic

Instruction Set

Mnemonic	Opcode	Description
NOP	00000	No operation
ADD	00001	Addition
SUB	00010	Subtraction
OR	00011	Logical OR
AND	00100	Logical AND
NOT	00101	Logical Complement
XOR	00110	Exclusive OR
CMP	00111	Arithmetic Comparison

Instruction Set

Mnemonic	Opcode	Description
Bxx	01000	Conditional Branch
JMP	01001	Jump
JMPL	01001	Jump and Link
LD	01010	Load direct from memory
LDI	01011	Load an immediate value
LDX	01100	Load indirect through reg + offset
ST	01101	Store direct to memory
STX	01110	Store indirect through reg + offset
HLT	11111	Halt
RETI	10000	Return from Interrupt

Instruction Format


	31...27	26...22	21...17	16	15...11	10...0
NOP	opcode	0...0				
ADD, SUB, OR, AND, XOR, CMP	opcode	rdst	rs1	0	rs2	0...0
ADD, SUB, OR, AND, XOR, CMP	opcode	rdst	rs1	1	immed16	
NOT	opcode	rdst	rs1	0...0		
MOV	opcode	rdst	rs1	1	0...0	

Instruction Format


	31...27	26...23	22	21...17	16	15...11
Bxx	opcode	Condition bits	immed23			
JMP	opcode	00000		rs1	0	immed16
JMPL	opcode	rdst		rs1	1	immed16
LD	opcode	rdst		immed22		
LDI	opcode	rdst		immed22		
LDX	opcode	rdst		rs1	immed17	
ST	opcode	rst		immed22		
STX	opcode	rst		rs1	immed17	
HLT	opcode	0...0				
RETI	opcode	00000		11111	0...0	

Branch Conditions


Cond	Mnemonic	Description
0000	BRA	Branch always
1000	BNV	Branch never
0001	BCC	Branch on carry clear
1001	BCS	Branch on carry set
0010	BVC	Branch on overflow clear
1010	BVS	Branch on overflow set
0011	BEQ	Branch on equal
1011	BNE	Branch on not equal
0100	BGE	Branch on greater than/equal to
1100	BLT	Branch on less than
0101	BGT	Branch on greater than
1101	BLE	Branch on less than/equal to
0110	BPL	Branch on plus
1110	BMI	Branch on minus

 

CPU Design

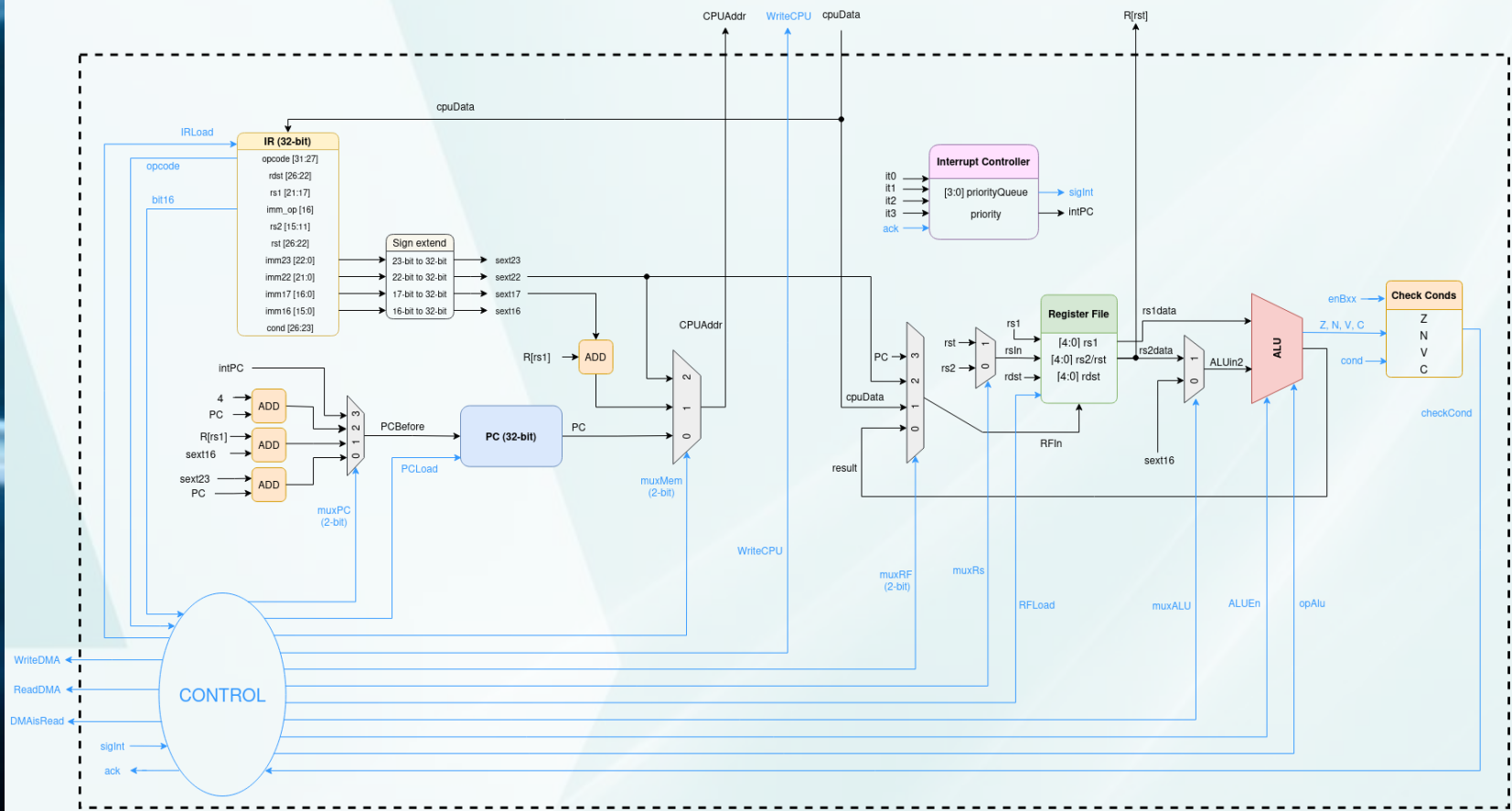

State Machine

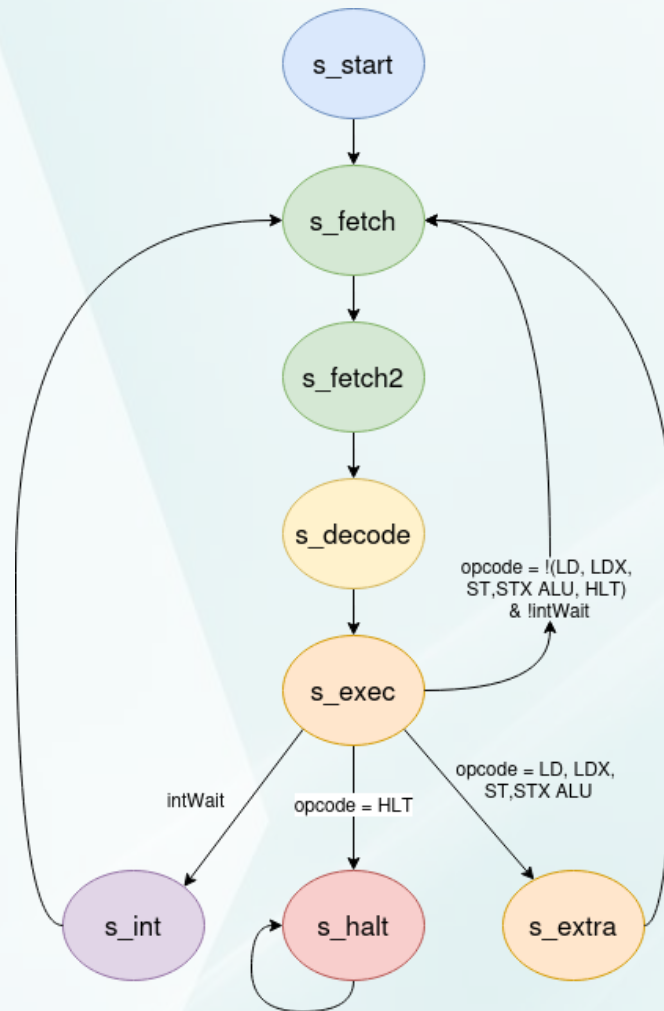


Control Signals


	Mux ALU	Mux Rs	Mux RF	Mux Mem	Mux PC	PC Load	RF Load	ALU En	Write CPU
ADD	0/1		0				1	1	
SUB	0/1		0				1	1	
OR	0/1		0				1	1	
AND	0/1		0				1	1	
NOT			0				1	1	
XOR	0/1		0				1	1	
CMP	0/1							1	
Bxx					0	1			
JMP					1	1	1		
JMPL			3		1	1			
LD			1	2			1		
LDI			2				1		
LDX			1	1			1		
ST		1		2					1
STX		1		1					1
NOP									
HLT									
RETI					1	1			

	mux RF	mux Mem	mux PC	PC Load	RF Load	IR Load	Read DMA	Write DMA
Fetch		1						
Fetch2			2	1		1		
Decode (dmaSwitch=0)							1	
Decode (dmaSwitch=1)								1
Int	3		3	1	1			


Memory Map

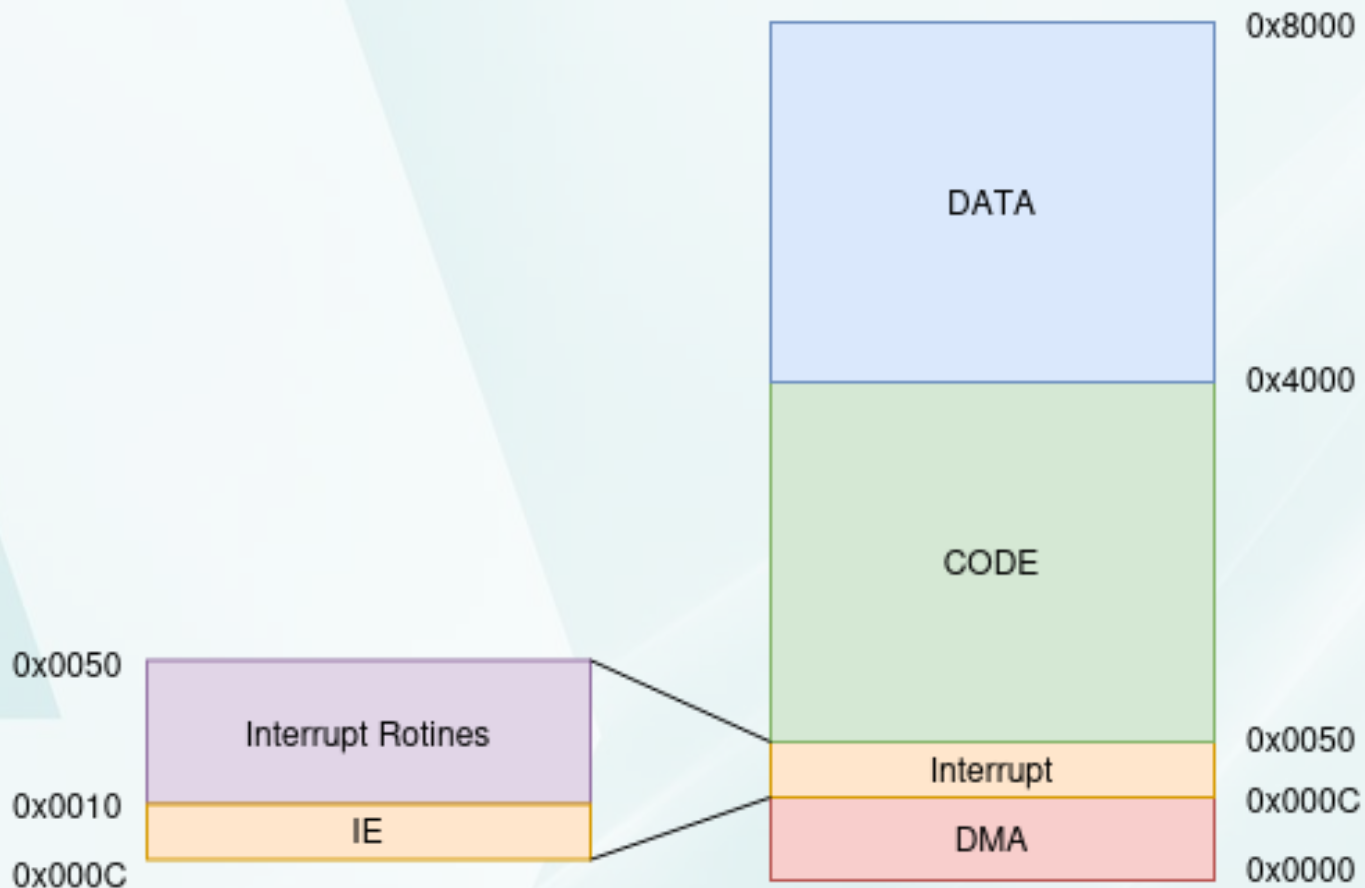


Memory IP Design

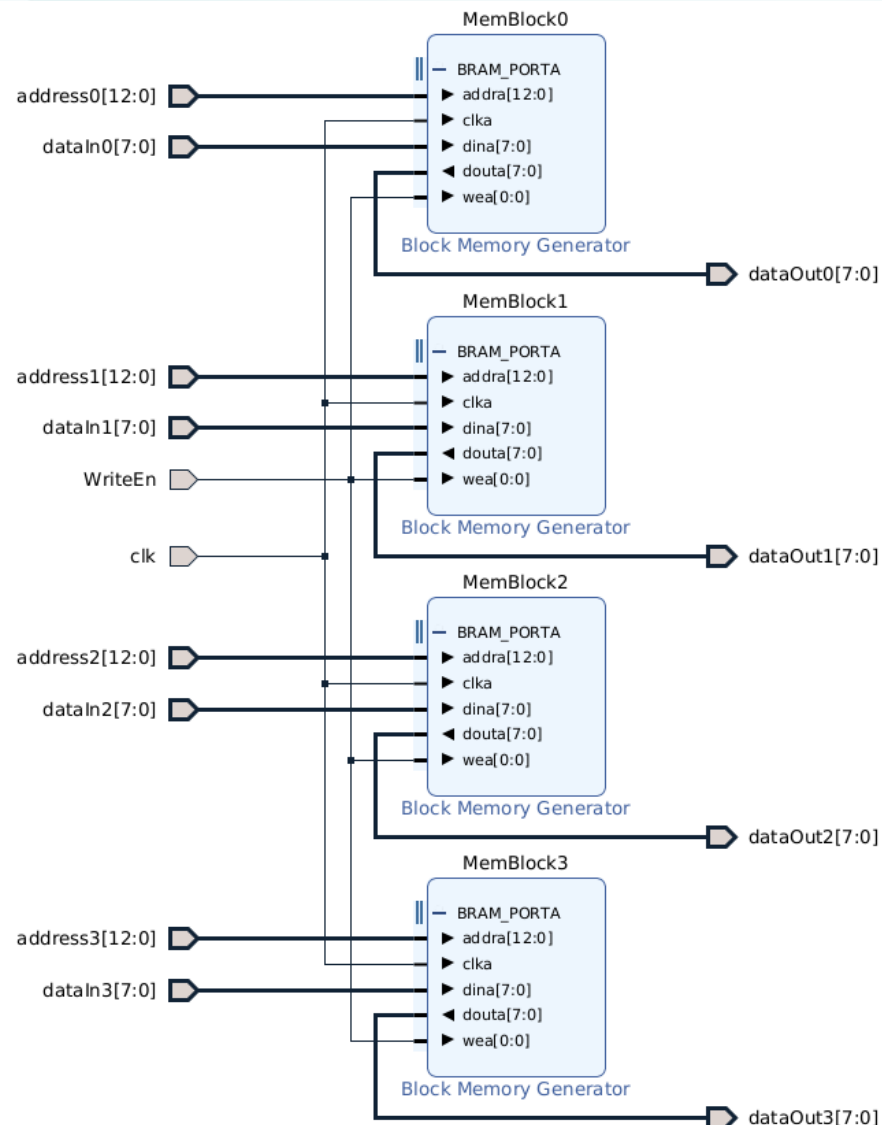

Register File IP Design

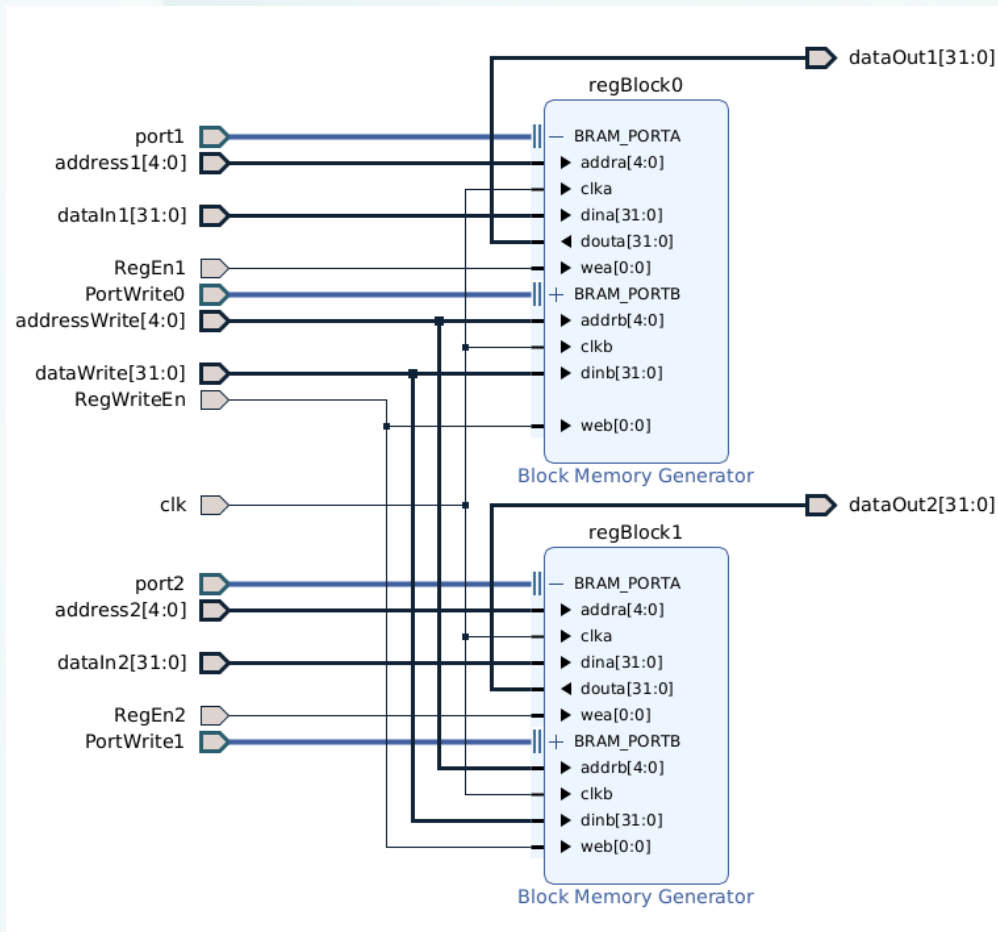

RTL Schematic

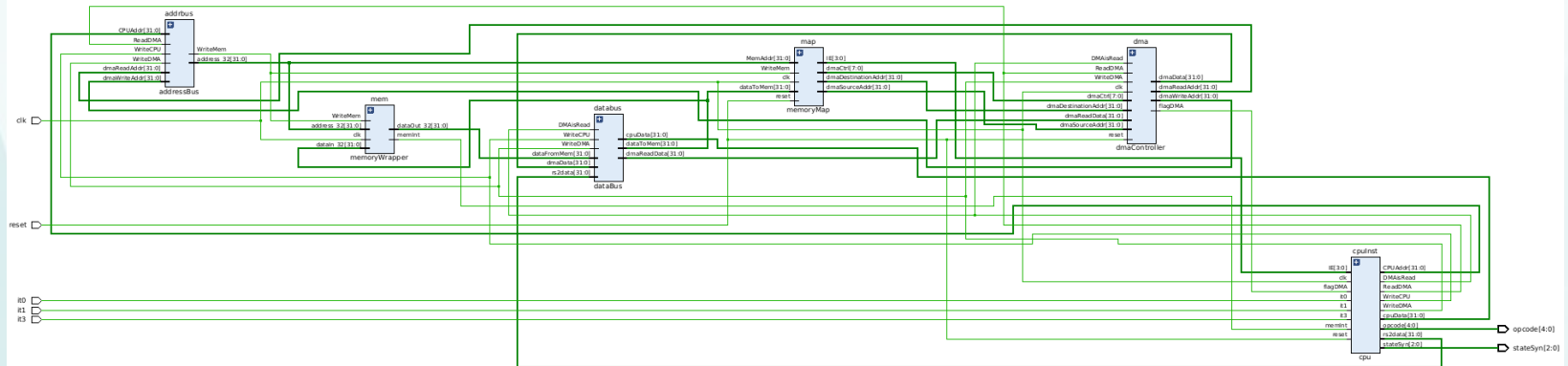


```
module top(  
    input clk,  
    input reset,  
    input it0,  
    input it1,  
    input it3,  
    output [2:0] stateSyn,  
    output [4:0] opcode  
);  
  
wire IRload, PCLoad, RFload, WriteCPU, bit16, ALUEn;  
wire [1:0] muxMem, muxRF, muxPC;  
wire [2:0] opAlu;  
wire [3:0] condBxxCu, IE;  
wire ack, sigInt;  
wire Z,N,C,V;  
wire clk_1hz;  
wire [7:0] dmaCtrl;  
wire [`MEM_DEPTH-1:0] intPC, address_32, CPUAddr;  
wire [`DATA_SIZE-1:0] rs2data, cpuData, dataIn_32, dataOut_32, dmaData, dmaRData;  
wire [`MEM_DEPTH-1:0] dmaWriteAddr, destinationAddr, sourceAddr, dmaRAddr;  
wire flagDMA, WriteMem, ReadDMA, WriteDMA, dmaSwitch, DMAisRead;  
  
cpu cpuInst (  
    .clk(clk),  
    .reset(reset),  
    .IE(IE),  
    .it0(it0),  
    .it1(it1),  
    .it3(it3),  
    .flagDMA(flagDMA),  
    .memInt(memInt),  
    .WriteCPU(WriteCPU),  
    .WriteDMA(WriteDMA),  
    .ReadDMA(ReadDMA),  
    .DMAisRead(DMAisRead),  
    .stateSyn(stateSyn),  
    .opcode(opcode),  
    .rs2data(rs2data),  
    .CPUAddr(CPUAddr),  
    .cpuData(cpuData)  
);
```

```
memoryWrapper mem (  
    .clk(clk),  
    .WriteMem(WriteMem),  
    .dataIn_32(dataIn_32),  
    .address_32(address_32),  
    .dataOut_32(dataOut_32),  
    .memInt(memInt)  
);  
  
addressBus addrbus (  
    .WriteCPU(WriteCPU),  
    .WriteDMA(WriteDMA),  
    .ReadDMA(ReadDMA),  
    .CPUAddr(CPUAddr),  
    .dmaWriteAddr(dmaWriteAddr),  
    .dmaReadAddr(dmaRAddr),  
    .WriteMem(WriteMem),  
    .address_32(address_32)  
);
```

```
dataBus databus(  
    .WriteCPU(WriteCPU),  
    .WriteDMA(WriteDMA),  
    .DMAisRead(DMAisRead),  
    .rs2data(rs2data),  
    .dmaData(dmaData),  
    .dataFromMem(dataOut_32),  
    .cpuData(cpuData),  
    .dmaReadData(dmaRData),  
    .dataToMem(dataIn_32)  
);
```

```
dmaController dma (  
    .clk(clk),  
    .reset(reset),  
    .ReadDMA(ReadDMA),  
    .DMAisRead(DMAisRead),  
    .WriteDMA(WriteDMA),  
    .dmaCtrl(dmaCtrl),  
    .dmaDestinationAddr(destinationAddr),  
    .dmaSourceAddr(sourceAddr),  
    .dmaReadData(dmaRData),  
    .dmaWriteAddr(dmaWriteAddr),  
    .dmaReadAddr(dmaRAddr),  
    .dmaData(dmaData),  
    .flagDMA(flagDMA)  
);  
  
memoryMap map (  
    .clk(clk),  
    .reset(reset),  
    .WriteMem(WriteMem),  
    .dataToMem(dataIn_32),  
    .MemAddr(address_32),  
    .dmaSourceAddr(sourceAddr),  
    .dmaDestinationAddr(destinationAddr),  
    .dmaCtrl(dmaCtrl),  
    .IE(IE)  
);  
endmodule
```

```
module cpu(  
    input clk,  
    input reset,  
    input [3:0] IE,  
    input it0,  
    input it1,  
    input it3,  
    input flagDMA,  
    input memInt,  
    output WriteCPU,  
    output WriteDMA,  
    output ReadDMA,  
    output DMAisRead,  
    output [2:0] stateSyn,  
    output [4:0] opcode,  
    output [`DATA_SIZE-1:0] rs2data,  
    output [`MEM_DEPTH-1:0] CPUAddr,  
    output [`DATA_SIZE-1:0] cpuData  
);  
  
wire [`MEM_DEPTH-1:0] intPC;  
wire [3:0] condBxxCu;  
wire [2:0] opAlu;  
wire [1:0] muxPC, muxMem, muxRF;  
wire muxALU, muxRs;  
wire ALUEn, IRLoad, PCLoad, RFLoad, bit16;  
wire Z, N, C, V;  
wire sigInt, ack;  
  
datapath dp(  
    .clk(clk),  
    .reset(reset),  
    .intPC(intPC),  
    .opAlu(opAlu),  
    .muxPC(muxPC),  
    .muxMem(muxMem),  
    .muxRF(muxRF),  
    .muxALU(muxALU),  
    .muxRs(muxRs),  
    .ALUEn(ALUEn),  
    .IRLoad(IRLoad),  
    .PCLoad(PCLoad),  
    .RFLoad(RFLoad),  
    .bit16(bit16),  
    .opcode(opcode),  
    .condBxxCu(condBxxCu),  
    .Z(Z),  
    .N(N),  
    .C(C),  
    .V(V),  
    .rs2data(rs2data),  
    .CPUAddr(CPUAddr),  
    .cpuData(cpuData)  
);
```

```
controlunit cu(  
    .clk(clk),  
    .reset(reset),  
    .opcode(opcode),  
    .bit16(bit16),  
    .sigInt(sigInt),  
    .condBxxCu(condBxxCu),  
    .Z(Z),  
    .N(N),  
    .C(C),  
    .V(V),  
    .flagDMA(flagDMA),  
    .muxPC(muxPC),  
    .muxMem(muxMem),  
    .muxRF(muxRF),  
    .muxALU(muxALU),  
    .muxRs(muxRs),  
    .ALUEn(ALUEn),  
    .IRLoad(IRLoad),  
    .PCLoad(PCLoad),  
    .RFLoad(RFLoad),  
    .WriteCPU(WriteCPU),  
    .WriteDMA(WriteDMA),  
    .ReadDMA(ReadDMA),  
    .DMAisRead(DMAisRead),  
    .opAlu(opAlu),  
    .stateSyn(stateSyn),  
    .ack(ack)  
);  
  
interruptController isr (  
    .clk(clk),  
    .reset(reset),  
    .IE(IE),  
    .it0(it0),  
    .it1(it1),  
    .it2(memInt),  
    .it3(it3),  
    .ack(ack),  
    .sigInt(sigInt),  
    .intPC(intPC)  
);  
  
endmodule
```

```
module datapath(
    input clk,
    input reset,
    input [`MEM_DEPTH-1:0] intPC,
    input [2:0] opAlu,
    input [1:0] muxPC,
    input [1:0] muxMem,
    input [1:0] muxRF,
    input muxALU,
    input muxRs,
    input ALUEn,
    input IRLoad,
    input PCLoad,
    input RFLoad,

    output bit16,
    output [4:0] opcode,
    output [3:0] condBxxCu,
    output Z,
    output N,
    output C,
    output V,
    output [`DATA_SIZE-1:0] rs2data,
    output [`MEM_DEPTH-1:0] CPUAddr,
    output [`DATA_SIZE-1:0] cpuData
);

reg [`DATA_SIZE-1:0] IR ;
reg [`MEM_DEPTH-1:0] PC ;
wire [`DATA_SIZE-1:0] result;

wire [4:0] rdst;           // destination register
wire [4:0] rst = IR[26:22]; // store register
wire [4:0] rs1 = IR[21:17]; // first operand register
wire [4:0] rs2 = IR[15:11]; // second operand register
wire [3:0] cond = IR[26:23]; // condition
wire [15:0] immed16 = IR[15:0]; // 16 bit immediate
wire [16:0] immed17 = IR[16:0]; // 17 bit immediate
wire [21:0] immed22 = IR[21:0]; // 22 bit immediate
wire [22:0] immed23 = IR[22:0]; // 23 bit immediate

wire [`DATA_SIZE-1:0] sext16, sext17, sext22, sext23;
wire [`MEM_DEPTH-1:0] nextPC;
wire [`DATA_SIZE-1:0] RFin;
wire [`DATA_SIZE-1:0] rs1data;
wire [4:0] rsIn;
wire [`DATA_SIZE-1:0] ALUin2;

assign rdst = (muxPC != 2'b11) ? IR[26:22] : 5'b11111;

assign sext16[`DATA_SIZE-1:0] = { ({`DATA_SIZE-16}{immed16[15]}) , immed16};
assign sext17[`DATA_SIZE-1:0] = { ({`DATA_SIZE-17}{immed17[16]}) , immed17};
assign sext22[`DATA_SIZE-1:0] = { ({`DATA_SIZE-22}{immed22[21]}) , immed22};
assign sext23[`DATA_SIZE-1:0] = { ({`DATA_SIZE-23}{immed23[22]}) , immed23};

always@(posedge clk) begin
    if (reset) begin
        IR <= 32'd0;
    end if (IRLoad) begin
        IR <= cpuData;
    end
end
```

```
assign nextPC = (muxPC == 2'd0) ? PC + sext23 :
                (muxPC == 2'd1) ? rs1data + sext16 :
                (muxPC == 2'd2) ? PC + 4 :
                (muxPC == 2'd3) ? intPC : 2'bx;

always@(posedge clk) begin
    if (reset) begin
        PC <= 32'h00000050;
    end if (PCLoad) begin
        PC <= nextPC;
    end
end

assign CPUAddr = (muxMem == 2'b00) ? PC :
                 (muxMem == 2'b01) ? rs1data + sext17 :
                 (muxMem == 2'b10) ? sext22 : 2'bx ;

assign RFin = (muxRF == 2'b00) ? result :
              (muxRF == 2'b01) ? cpuData :
              (muxRF == 2'b10) ? sext22 :
              (muxRF == 2'b11) ? PC : 2'bx;

assign rsIn = (muxRs == 1'b0) ? rs2 :
              (muxRs == 1'b1) ? rst : 1'bx;

RegFileHandler RF(
    .clk(clk),
    .writeRF(RFLoad),
    .readAddr1(rs1),
    .readAddr2(rsIn),
    .writeAddr(rdst),
    .writeData(RFin),
    .readData1(rs1data),
    .readData2(rs2data)
);

assign ALUin2 = (muxALU == 1'b0) ? sext16 :
                (muxALU == 1'b1) ? rs2data : 1'bx;

alu al (
    .ALUEn(ALUEn),
    .opAlu(opAlu),
    .IN1(rs1data),
    .IN2(ALUin2),
    .Z(Z),
    .N(N),
    .C(C),
    .V(V),
    .result(result)
);

assign condBxxCu = cond;
assign opcode = IR[31:27];
assign bit16 = IR[16];
```

ALU


```
`define ADD_ (opAlu == 1)
`define SUB_ (opAlu == 2)
`define OR_ (opAlu == 3)
`define AND_ (opAlu == 4)
`define NOT_ (opAlu == 5)
`define XOR_ (opAlu == 6)
`define CMP_ (opAlu == 7)
`define ALUflags (`ADD_||`SUB_||`CMP_)
`define WIDTH 32
```

```
assign {carryAux, resultAux} = (`ADD_) ? IN1 + IN2 :
                                (`SUB_) ? IN1 - IN2 :
                                (`OR_) ? IN1 | IN2 :
                                (`AND_) ? IN1 & IN2 :
                                (`NOT_) ? ~IN1 :
                                (`XOR_) ? IN1 ^ IN2 :
                                (`CMP_) ? IN1 - IN2 : 0;

assign {carry, result} = (ALUEn) ? {carryAux, resultAux} : 0;

assign sigSubb = (`SUB_) ? 1'b1 : 1'b0;

always @(*) begin
    if (ALUEn && ALUflags) begin
        Z <= ~(|result[`WIDTH-1:0]);
        C <= carry;
        N <= result[`WIDTH-1];
        V <= (result[`WIDTH-1] & ~IN1[`WIDTH-1] & ~(sigSubb ^ IN2[`WIDTH-1])) |
              (~result[`WIDTH-1] & IN1[`WIDTH-1] & (sigSubb ^ IN2[`WIDTH-1]));
    end
end
```

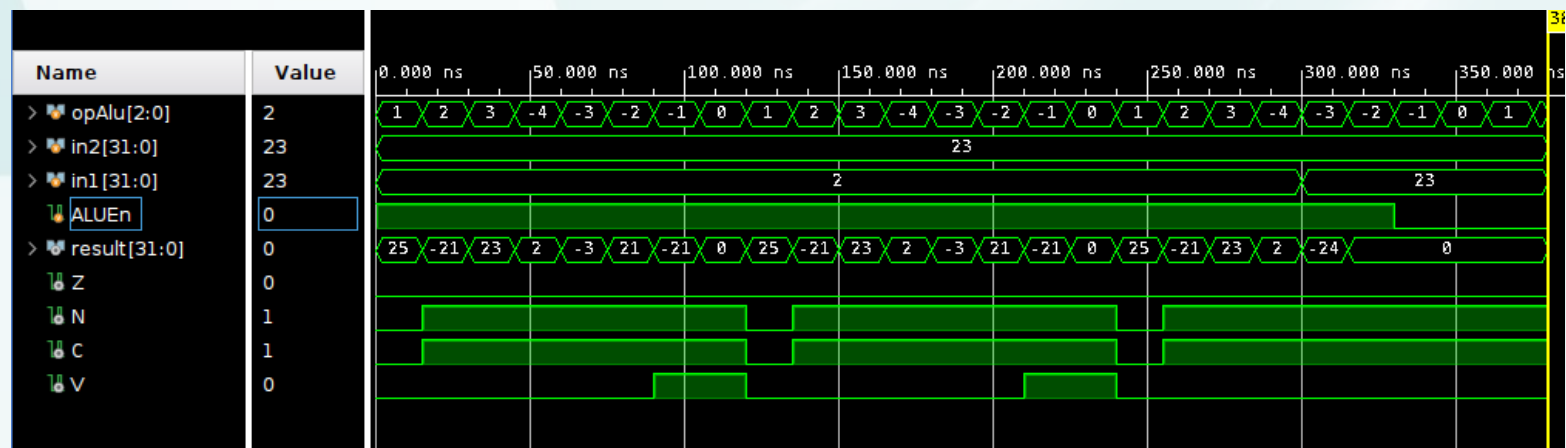

Test Bench Register File


```
`define REG_WIDTH 32
`define REG_DEPTH 5

module RegFileHandler(
    input    clk,
    input    WriteRF,
    input    [`REG_DEPTH-1:0] readAddr1,
    input    [`REG_DEPTH-1:0] readAddr2,
    input    [`REG_DEPTH-1:0] writeAddr,
    input    [`REG_WIDTH-1:0] writeData,
    output   [`REG_WIDTH-1:0] readData1,
    output   [`REG_WIDTH-1:0] readData2
);

    RegFileIP regInst(
        .clk(clk),
        .address1(readAddr1),
        .address2(readAddr2),
        .RegWriteEn(WriteRF),
        .addressWrite(writeAddr),
        .dataWrite(writeData),
        .dataOut1(readData1),
        .dataOut2(readData2)
    );

endmodule
```

Name	Value
clk	1
writeEn	1
> readAddr1[31:0]	00000003
> readAddr2[31:0]	00000007
> writeAddr[31:0]	00000003
> writeData[31:0]	00000378
> readData1[31:0]	00000378
> readData2[31:0]	0000006f

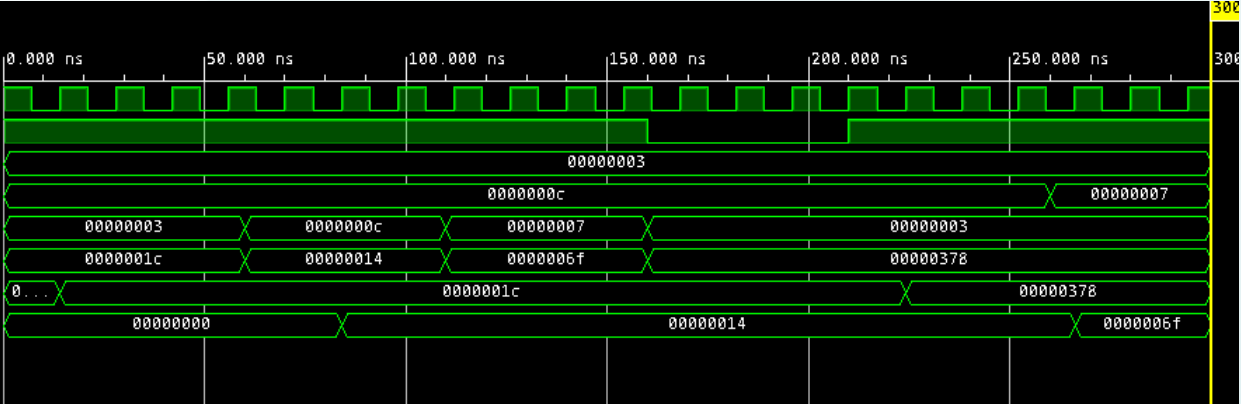

```
module controlunit(
    input clk,
    input reset,
    input [4:0] opcode,
    input bit16,
    input sigInt,
    input [3:0] condBxxCu,
    input Z,
    input N,
    input C,
    input V,
    input flagDMA,

    output [1:0] muxPC,
    output [1:0] muxMem,
    output [1:0] muxRF,
    output muxALU,
    output muxRs,
    output ALUEn,
    output IRLoad,
    output PCLoad,
    output RFLoad,
    output WriteCPU,
    output WriteDMA,
    output ReadDMA,
    output DMAIsRead,
    output [2:0] opAlu,
    output [2:0] stateSyn,
    output ack
);

parameter s_start = 5'd0, s_fetch = 5'd1, s_fetch2 = 5'd2, s_decode = 5'd3,
s_exec = 5'd4, s_extra = 5'd5, s_halt = 5'd6, s_int = 5'd7;

reg [3:0] state;
wire enBxx;
reg dmaSwitch;
reg intProc;
reg intWait;

always @(posedge clk) begin
    if (reset == 1'b1) begin
        state <= s_start;
        intProc <= 0;
        intWait <= 0;
        dmaSwitch <= 1;
    end
    else begin
        case (state)
            s_start:
                state <= s_fetch;
            s_fetch:
                if (flagDMA) begin
                    dmaSwitch <= dmaSwitch + 1;
                    state <= s_fetch2;
                end
                else begin
                    state <= s_fetch2;
                end
            s_fetch2:
                state <= s_decode;
            s_decode:
                state <= s_exec;
            s_exec:
                if ('HLT) begin
                    state <= s_halt;
                end
                else if ('LD||'LDX||'ALU||'ST||'STX) begin
                    state <= s_extra;
                end
                else if (intWait) begin
                    intWait <= 0;
                    intProc <= 1;
                    state <= s_int;
                end
                else begin
                    state <= s_fetch;
                end
        endcase
    end
end
```

```
s_extra:
    if (intWait) begin
        intWait <= 0;
        intProc <= 1;
        state <= s_int;
    end
    else begin
        state <= s_fetch;
    end
end
s_halt:
    state <= s_halt;
s_int:
    state <= s_fetch;
default:
    state <= s_start;
endcase

if (sigInt) begin
    if (intProc == 0 && intWait == 0) begin
        intWait <= 1;
    end
end
end
end

assign muxRs = (('ST || 'STX) && (state == s_exec || state == s_extra)) ? 1'd1 : 1'd0;
assign muxALU = (bit16 && ('ALU) && (state == s_exec)) ? 1'b0 : 1'b1;

assign muxPC = ('Bxx && (state == s_exec)) ? 2'd0 :
(('JMP || 'JMP||'RET||'RET) && (state == s_exec)) ? 2'd1 :
(state == s_fetch2) ? 2'd2 :
(state == s_int) ? 2'd3 : 2'b10;

assign muxMem = (('LD || 'ST) && (state == s_exec) || ('ST && state == s_extra)) ? 2'd2 :
(('LDX || 'STX) && (state == s_exec) || ('STX && state == s_extra)) ? 2'd1 :
(state == s_fetch) ? 2'd0 : 2'bx;

assign muxRF = (('ALU) && (state == s_exec)) ? 2'd0 :
(('LDX || 'LD) && ((state == s_exec) || state == s_extra)) ? 2'd1 :
(('LDI) && (state == s_exec)) ? 2'd2 :
(('JMPL) && (state == s_exec) || (state == s_int) ? 2'd3 : 2'bx;

assign ALUEn = ('ALU && (state == s_exec)) ? 1'd1 : 1'd0;
assign IRLoad = (state == s_fetch2) ? 1'd1 : 1'd0;
assign PCLoad = (((('Bxx && checkCond) || 'JMP || 'JMPL||'RET) && (state == s_exec)) ||
state == s_fetch2 || (state == s_int)) ? 1'd1 : 1'd0;
assign RFLoad = (('ADD||'SUB||'OR||'AND||'NOT||'XOR||'JMPL||'LD||'LDX) && state == s_exec) ||
('LD || 'LDX) && (state == s_extra) || (state == s_int) ? 1'd1 : 1'd0;
assign WriteCPU = (('ST || 'STX) && (state == s_exec || state == s_extra)) ? 1'd1 : 1'd0;

assign ReadDMA = (flagDMA && (state == s_decode) && dmaSwitch == 0) ? 1'd1 : 1'd0;
assign DMAIsRead = (flagDMA && state == s_exec && dmaSwitch == 0) ? 1'd1 : 1'd0;
assign WriteDMA = (flagDMA && state == s_decode && dmaSwitch == 1) ? 1'd1 : 1'd0;

assign enBxx = (opcode == 8) ? 1'b1 : 1'b0;
assign opAlu = ('ALU && (state == s_exec)) ? opcode[2:0] : 0;
assign stateSyn = state;

assign ack = (intProc && 'RET) ? 1'd1 : 1'd0;

checkCondition ccond(
    .enBxx(enBxx),
    .cond(condBxxCu),
    .Z(Z),
    .N(N),
    .C(C),
    .V(V),
    .checkCond(checkCond)
);
```

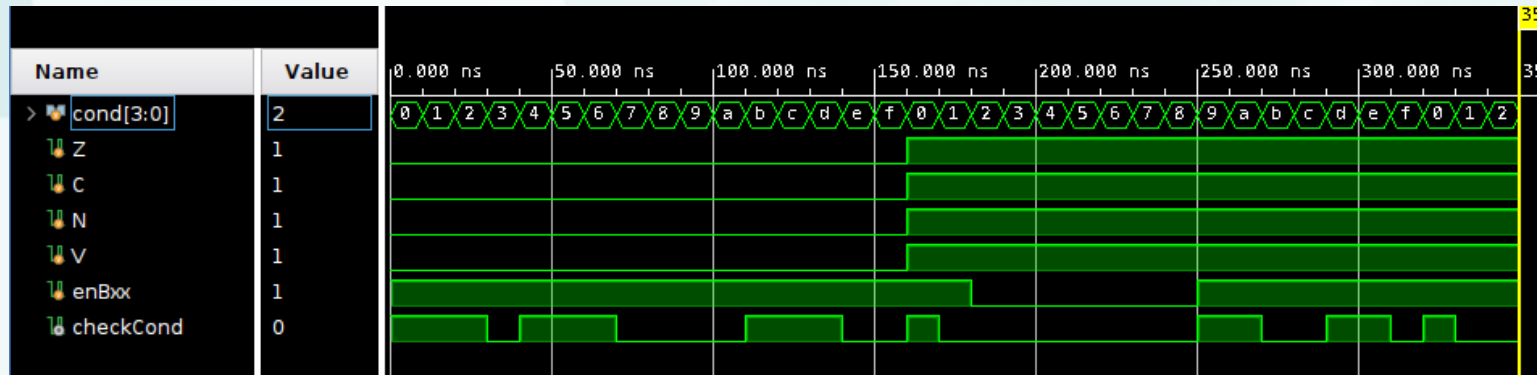

Test Bench CheckCond



```
`define BRA 4'b0000 // 0: always
`define BNV 4'b1000 // 8: never
`define BCC 4'b0001 // 1: carry clear
`define BCS 4'b1001 // 9: carry set
`define BVC 4'b0010 // 2: overflow clear
`define BVS 4'b1010 // a: overflow set
`define BEQ 4'b0011 // 3: equal
`define BNE 4'b1011 // b: not equal
`define BGE 4'b0100 // 4: greater than/ equal to
`define BLT 4'b1100 // c: less than
`define BGT 4'b0101 // 5: greater than
`define BLE 4'b1101 // d: less than/ equal to
`define BPL 4'b0110 // 6: on plus
`define BMI 4'b1110 // e: on minus
```

```
assign checkCondAux = (cond == `BRA) ? 1'd1 :
                      (cond == `BNV) ? 1'd0 :
                      (cond == `BCC) ? ~C :
                      (cond == `BCS) ? C :
                      (cond == `BVC) ? ~V :
                      (cond == `BVS) ? V :
                      (cond == `BEQ) ? Z :
                      (cond == `BNE) ? ~Z :
                      (cond == `BGE) ? (N & V) | (~N & ~V) :
                      (cond == `BLT) ? ~(N & V) | (~N & ~V) :
                      (cond == `BGT) ? ~Z & ((N & V) | (~N & ~V)) :
                      (cond == `BLE) ? Z | ((N & V) | (~N & ~V)) :
                      (cond == `BPL) ? ~N :
                      (cond == `BMI) ? N : 1'b0;

assign checkCond = enBxx ? checkCondAux : 1'b0;
```




Interrupt Controller

```
module interruptController(  
    input clk,  
    input reset,  
    input [3:0] IE,  
    input it0,  
    input it1,  
    input it2,  
    input it3,  
    input ack,  
  
    output reg sigInt,  
    output reg ['MEM_DEPTH-1:0] intPC  
);  
    reg [3:0] priorityQueue;  
    reg [1:0] priority;  
  
    always @(posedge clk) begin  
        if (reset) begin  
            priorityQueue <= 4'b0000;  
        end else if (ack) begin  
            priorityQueue[priority] <= 1'b0;  
        end  
    end  
  
    always @* begin  
        if (priorityQueue != 4'b0000) begin  
            if (priorityQueue[3]) begin  
                intPC <= 32'h00000010;  
                priority <= 3;  
            end else if (priorityQueue[2]) begin  
                intPC <= 32'h00000020;  
                priority <= 2;  
            end else if (priorityQueue[1]) begin  
                intPC <= 32'h00000030;  
                priority <= 1;  
            end else if (priorityQueue[0]) begin  
                intPC <= 32'h00000040;  
                priority <= 0;  
            end else begin  
                intPC <= 32'bx;  
            end  
            sigInt <= 1'b1;  
        end else begin  
            sigInt <= 1'b0;  
            intPC <= 32'bx;  
            priority <= 1'bx;  
        end  
        priorityQueue <= priorityQueue | {it3 & IE[3], it2 & IE[2], it1 & IE[1], it0 & IE[0]};  
    end  
endmodule
```

Interrupt	Priority	Interrupt Enable	intPC
it0	0	IE[0]	0x10
it1	1	IE[1]	0x20
it2	2	IE[2]	0x30
it3	3	IE[3]	0x40


Test Bench InterruptController

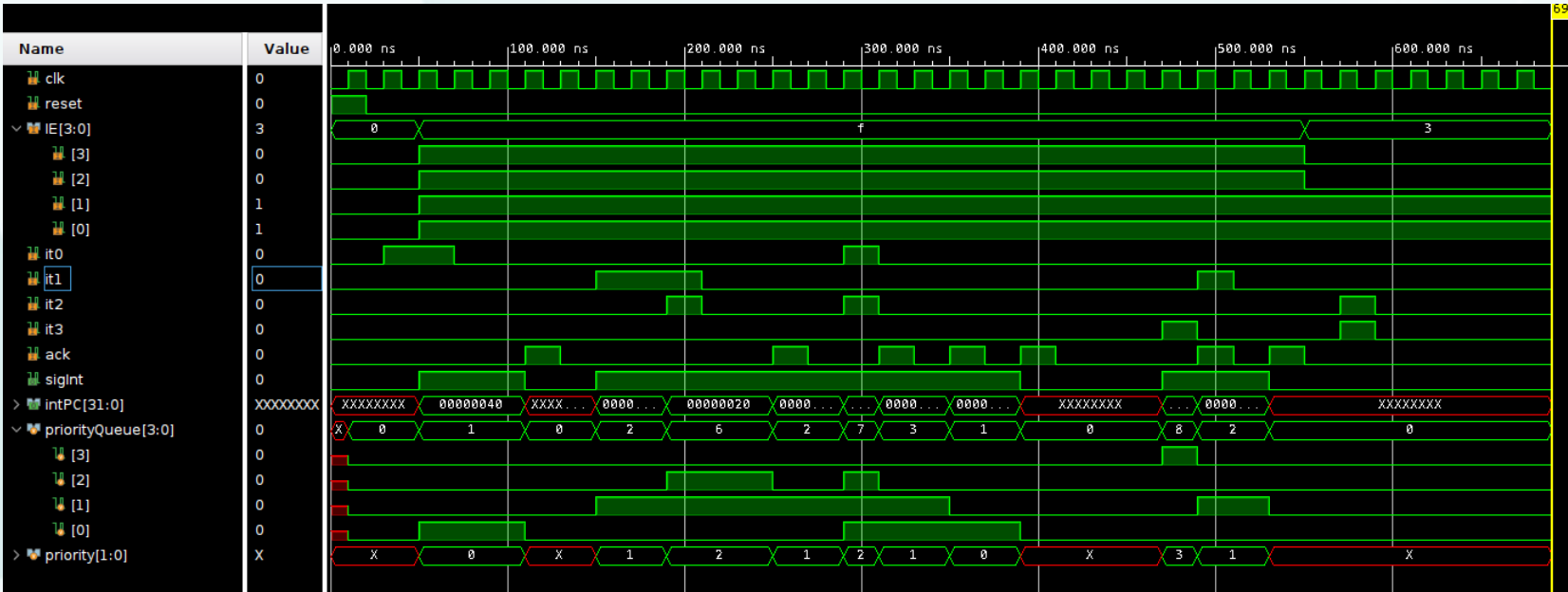

```
module memoryWrapper(  
    input clk,  
    input WriteMem,  
    input [`MEM_WIDTH-1:0]dataIn_32,  
    input [`MEM_DEPTH-1:0]address_32,  
    output [`MEM_WIDTH-1:0]dataOut_32,  
    output memInt  
);  
  
wire [`REAL_MEM_SIZE-1:0] address_15 = address_32[`REAL_MEM_SIZE-1:0];  
wire [`REAL_MEM_DEPTH-1:0] address0;  
wire [`REAL_MEM_DEPTH-1:0] address1;  
wire [`REAL_MEM_DEPTH-1:0] address2;  
wire [`REAL_MEM_DEPTH-1:0] address3;  
  
wire [`MEM_WIDTH-1:0] dataIn0;  
wire [`MEM_WIDTH-1:0] dataIn1;  
wire [`MEM_WIDTH-1:0] dataIn2;  
wire [`MEM_WIDTH-1:0] dataIn3;  
  
wire [`IP_WIDTH-1:0] dataOut0;  
wire [`IP_WIDTH-1:0] dataOut1;  
wire [`IP_WIDTH-1:0] dataOut2;  
wire [`IP_WIDTH-1:0] dataOut3;  
  
reg bit0;  
reg bit1;  
wire [`MEM_WIDTH-1:0] dataInput;  
wire WriteMemCond;  
  
assign WriteMemCond = ((address_32[`REAL_MEM_SIZE-1] & WriteMem &  
    ~|address_32[`MEM_DEPTH-1:`REAL_MEM_SIZE]) |  
    (~|address_32[`MEM_WIDTH-1:4] & WriteMem));  
assign memInt = (~WriteMemCond & WriteMem);  
  
always @(*) begin  
    if (address_15[0] == 1'b1 || address_15[0] == 1'b0) begin  
        bit0 <= address_15[0];  
        bit1 <= address_15[1];  
    end  
end
```

```
assign address0 = (bit1 | bit0) ? address_15[`REAL_MEM_SIZE-1:2]+1 : address_15[`REAL_MEM_SIZE-1:2];  
assign address1 = (bit1) ? address_15[`REAL_MEM_SIZE-1:2]+1 : address_15[`REAL_MEM_SIZE-1:2];  
assign address2 = (bit1 & bit0) ? address_15[`REAL_MEM_SIZE-1:2]+1 : address_15[`REAL_MEM_SIZE-1:2];  
assign address3 = address_15[`REAL_MEM_SIZE-1:2];  
  
assign dataInput = (~bit1 & ~bit0) ? {dataIn_32[31:24], dataIn_32[23:16], dataIn_32[15:8], dataIn_32[7:0]} :  
    (~bit1 & bit0) ? {dataIn_32[23:16], dataIn_32[15:8], dataIn_32[7:0], dataIn_32[31:24]} :  
    (bit1 & ~bit0) ? {dataIn_32[15:8], dataIn_32[7:0], dataIn_32[31:24], dataIn_32[23:16]} :  
    (bit1 & bit0) ? {dataIn_32[7:0], dataIn_32[31:24], dataIn_32[23:16], dataIn_32[15:8]} :  
    32'b0;  
  
assign dataIn0 [`MEM_WIDTH-1:0] = dataInput[31:24];  
assign dataIn1 [`MEM_WIDTH-1:0] = dataInput[23:16];  
assign dataIn2 [`MEM_WIDTH-1:0] = dataInput[15:8];  
assign dataIn3 [`MEM_WIDTH-1:0] = dataInput[7:0];  
  
assign dataOut_32 = (~bit1 & ~bit0) ? {dataOut0, dataOut1, dataOut2, dataOut3} :  
    (~bit1 & bit0) ? {dataOut1, dataOut2, dataOut3, dataOut0} :  
    (bit1 & ~bit0) ? {dataOut2, dataOut3, dataOut0, dataOut1} :  
    (bit1 & bit0) ? {dataOut3, dataOut0, dataOut1, dataOut2} : 32'b0;  
  
memory_ip memIP (  
    .WriteEn(WriteMemCond),  
    .address0(address0),  
    .address1(address1),  
    .address2(address2),  
    .address3(address3),  
    .clk(clk),  
    .dataIn0(dataIn0),  
    .dataIn1(dataIn1),  
    .dataIn2(dataIn2),  
    .dataIn3(dataIn3),  
    .dataOut0(dataOut0),  
    .dataOut1(dataOut1),  
    .dataOut2(dataOut2),  
    .dataOut3(dataOut3)  
);
```

Test Bench Memory

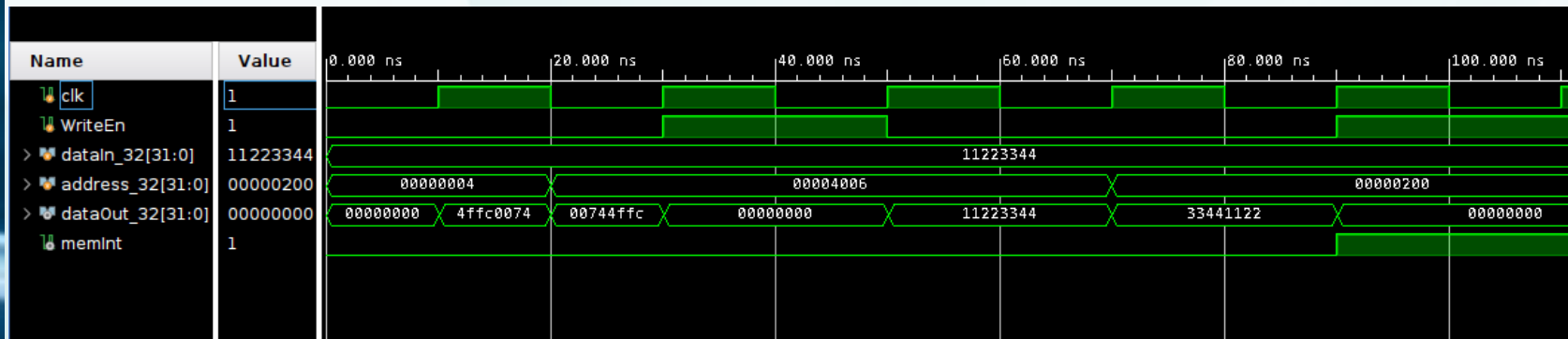

```
`define MEM_DEPTH 32
`define DATA_SIZE 32

// the Address Bus is responsible for selecting the appropriate memory address based on the control signals
module addressBus(
    input WriteCPU,           // cpu memory write enable signal
    input WriteDMA,           // dma memory write enable signal
    input ReadDMA,            // dma memory read enable signal
    input [`MEM_DEPTH-1:0] CPUAddr, // cpu memory address to read or write
    input [`MEM_DEPTH-1:0] dmaWriteAddr, // dma memory address to write
    input [`MEM_DEPTH-1:0] dmaReadAddr, // dma memory address to read

    output WriteMem,          // memory write enable signal
    output [`MEM_DEPTH-1:0] address_32 // memory address
);

    assign address_32 = (WriteCPU == 1) ? CPUAddr :
    | (WriteDMA == 1) ? dmaWriteAddr :
    | (ReadDMA == 1) ? dmaReadAddr : CPUAddr;

    assign WriteMem = ((WriteCPU != WriteDMA) && ReadDMA == 0) ? 1 : 0;
endmodule
```


```
`define MEM_DEPTH 32
`define DATA_SIZE 32

// the Data Bus is responsible for selecting the appropriate data to write in the memory
// and attributing the data read from the memory to the appropriate variable (dmaRead or cpuData)
module dataBus(
    input WriteCPU,                // cpu memory write enable signal
    input WriteDMA,                // dma memory write enable signal
    input DMAisRead,              // dma read signal (ReadDMA cant be enabled on s_exec)
    input [`DATA_SIZE-1:0] rs2data, // cpu data to write in memory
    input [`DATA_SIZE-1:0] dmaData,  // dma data to write in memory
    input [`DATA_SIZE-1:0] dataFromMem, // memory data to be read by cpu or dma


    output [`DATA_SIZE-1:0] cpuData, // cpu data to be read from memory
    output [`DATA_SIZE-1:0] dmaReadData, // dma data to be read from memory
    output [`DATA_SIZE-1:0] dataToMem // data to write in memory
);

    assign dataToMem = (WriteCPU == 1) ? rs2data :
    | | | | | (WriteDMA == 1) ? dmaData : 32'bx;

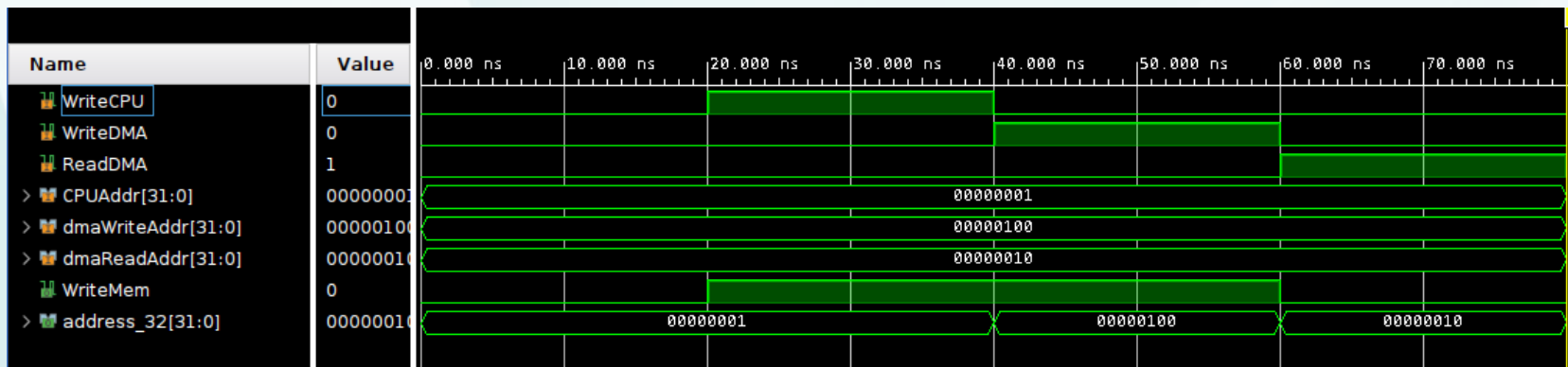    assign dmaReadData = (DMAisRead == 1) ? dataFromMem : 32'bx;
    assign cpuData = (DMAisRead == 0) ? dataFromMem : 32'bx;
endmodule
```



Test Bench DataBus

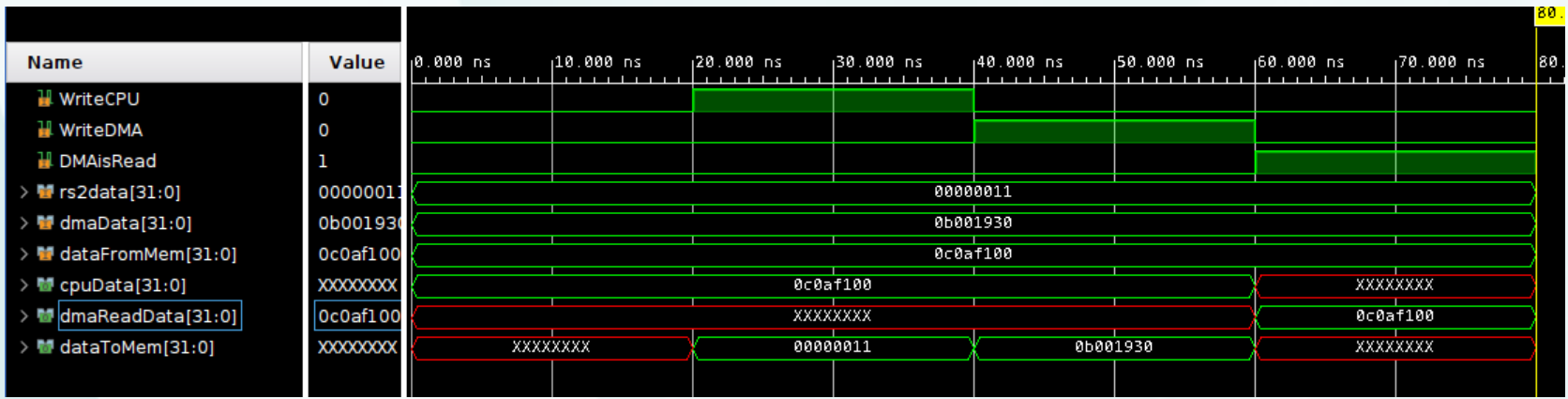

```
`define DATA_SIZE 32
`define MEM_DEPTH 32
`define S_IDLE 0
`define S_TRANSFER 1
`define S_END 2


module dmaController(
    input clk,
    input reset,
    input ReadDMA,
    input DMAisRead,
    input WriteDMA,
    input [7:0] dmaCtrl,
    input [`MEM_DEPTH-1:0] dmaDestinationAddr,
    input [`MEM_DEPTH-1:0] dmaSourceAddr,
    input [`DATA_SIZE-1:0] dmaReadData,
    output reg [`MEM_DEPTH-1:0] dmaWriteAddr,
    output reg [`MEM_DEPTH-1:0] dmaReadAddr,
    output reg [`DATA_SIZE-1:0] dmaData,
    output reg flagDMA
);

    reg [7:0] counter;
    reg [1:0] state;
    wire start = dmaCtrl[7];
    wire [6:0] transferLength = dmaCtrl[6:0];

    always @(*) begin
        if (flagDMA && DMAisRead) begin
            dmaData <= dmaReadData;
        end
    end
end
```

```
always @(posedge clk) begin
    if (reset) begin
        state <= `S_IDLE;
    end else begin
        case(state)
            `S_IDLE: begin
                flagDMA <= 2'b0;
                if (start == 1) begin
                    state <= `S_TRANSFER;
                    counter <= 8'h00;
                    dmaWriteAddr <= dmaDestinationAddr - 4;
                    dmaReadAddr <= dmaSourceAddr;
                end
            end
            `S_TRANSFER: begin
                if (counter < transferLength) begin
                    flagDMA <= 1;
                    if (ReadDMA) begin
                        dmaWriteAddr = dmaWriteAddr + 4;
                        dmaReadAddr = dmaReadAddr + 4;
                    end
                    if (WriteDMA) begin
                        counter <= counter + 1;
                    end
                end else begin
                    state <= `S_END;
                end
            end
            `S_END: begin
                state <= `S_IDLE;
                flagDMA <= 0;
                counter <= 0;
            end
        endcase
    end
end
endmodule
```

Test Bench DMA Controller

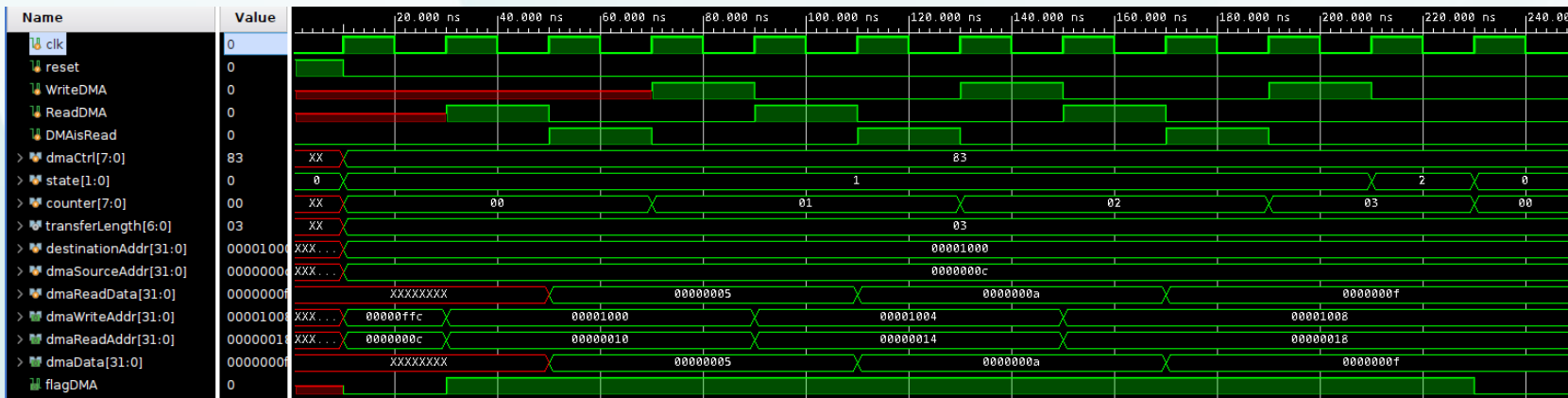




Memory Mapping



```
module memoryMap (  
    input clk,  
    input reset,  
    input WriteMem,  
    input [`DATA_SIZE-1:0]dataToMem,  
    input [`MEM_DEPTH-1:0]MemAddr,  
    output reg [`MEM_DEPTH-1:0]dmaSourceAddr,  
    output reg [`MEM_DEPTH-1:0]dmaDestinationAddr,  
    output [7:0]dmaCtrl,  
    output [3:0]IE  
);  
  
    // memory write enable signal  
    // data to write in memory  
    // memory address  
    // dma source address  
    // dma destination address  
    // dma control "register"  
    // interrupt enable  
  
    reg [`MEM_DEPTH-1:0]dmaCtrlAddr;  
    reg [`MEM_DEPTH-1:0]dmaSource;  
    reg [`MEM_DEPTH-1:0]dmaDestination;  
    reg [`DATA_SIZE-1:0]dmaReg;  
    reg [`MEM_DEPTH-1:0]interruptCtrlAddr;  
    reg [`DATA_SIZE-1:0]interruptCtrl;  
  
    assign IE = interruptCtrl [3:0];  
    assign dmaCtrl = dmaReg[7:0];  
  
    always @(posedge clk) begin  
        if (reset) begin  
            dmaCtrlAddr <= 32'h00000000;  
            dmaSource <= 32'h00000004;  
            dmaDestination <= 32'h00000008;  
            interruptCtrlAddr <= 32'h0000000c;  
  
            dmaDestinationAddr <= 32'h00004100;  
            dmaSourceAddr <= 32'h00000050;  
            dmaReg <= 32'h00000000;  
            interruptCtrl <= 32'h00000000;  
        end  
    end  
  
    always @(*) begin  
        if (WriteMem) begin  
            case (MemAddr)  
                dmaCtrlAddr:  
                    dmaReg <= dataToMem;  
                dmaSource:  
                    dmaSourceAddr <= dataToMem;  
                dmaDestination:  
                    dmaDestinationAddr <= dataToMem;  
                interruptCtrlAddr:  
                    interruptCtrl <= dataToMem;  
                default:  
                    ;  
            endcase  
        end  
    end  
endmodule
```

Test Bench MemoryMap

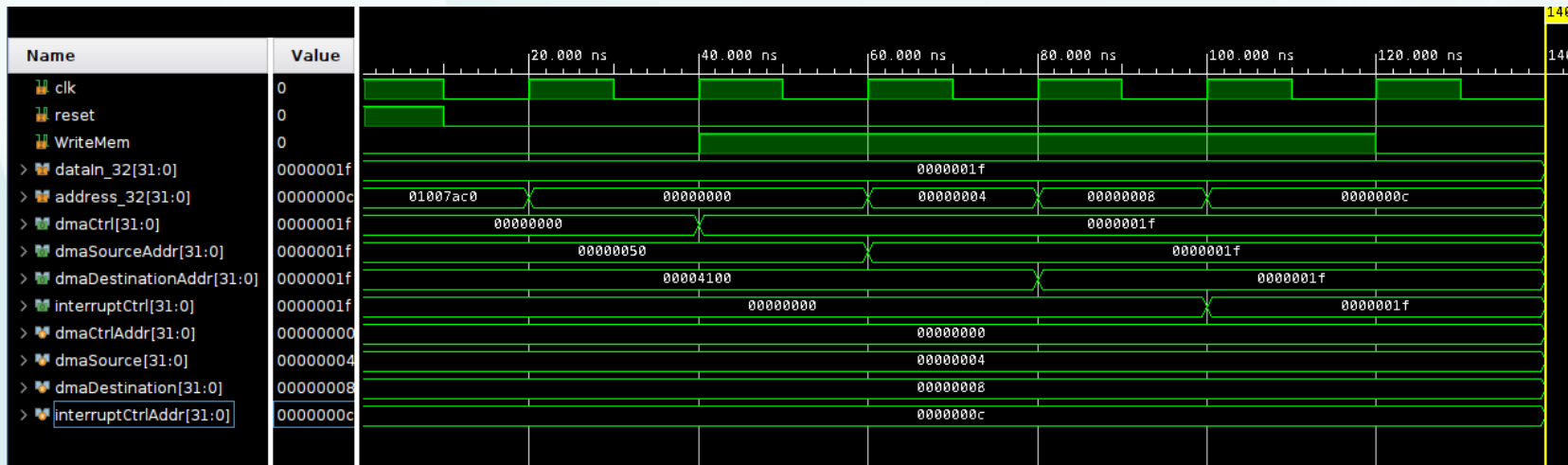

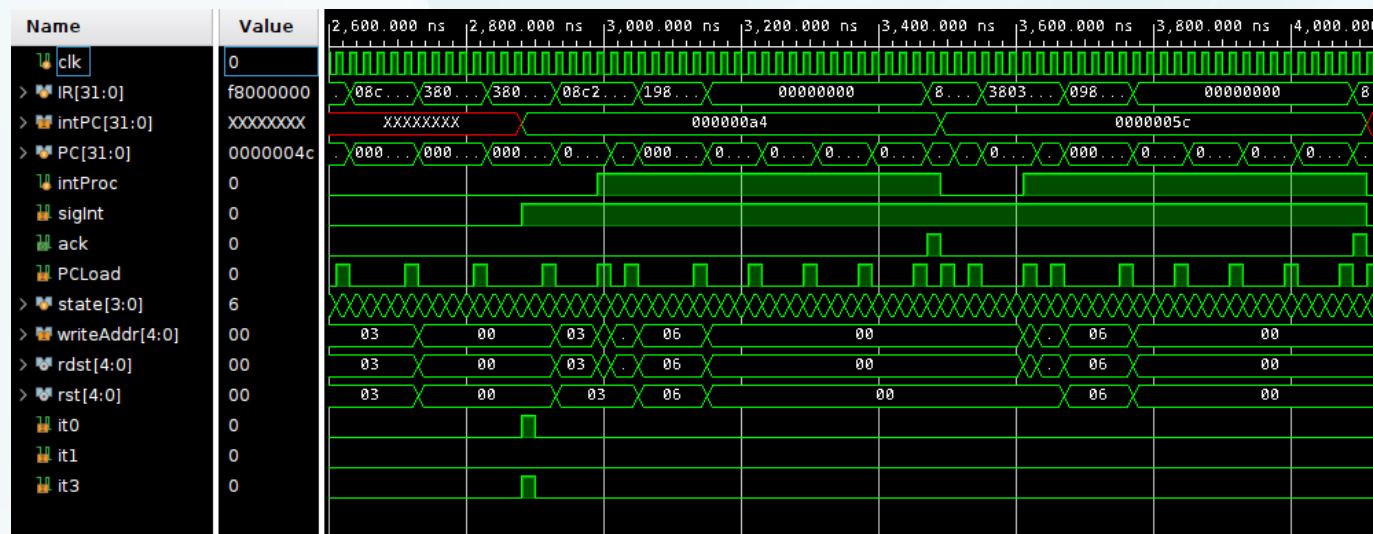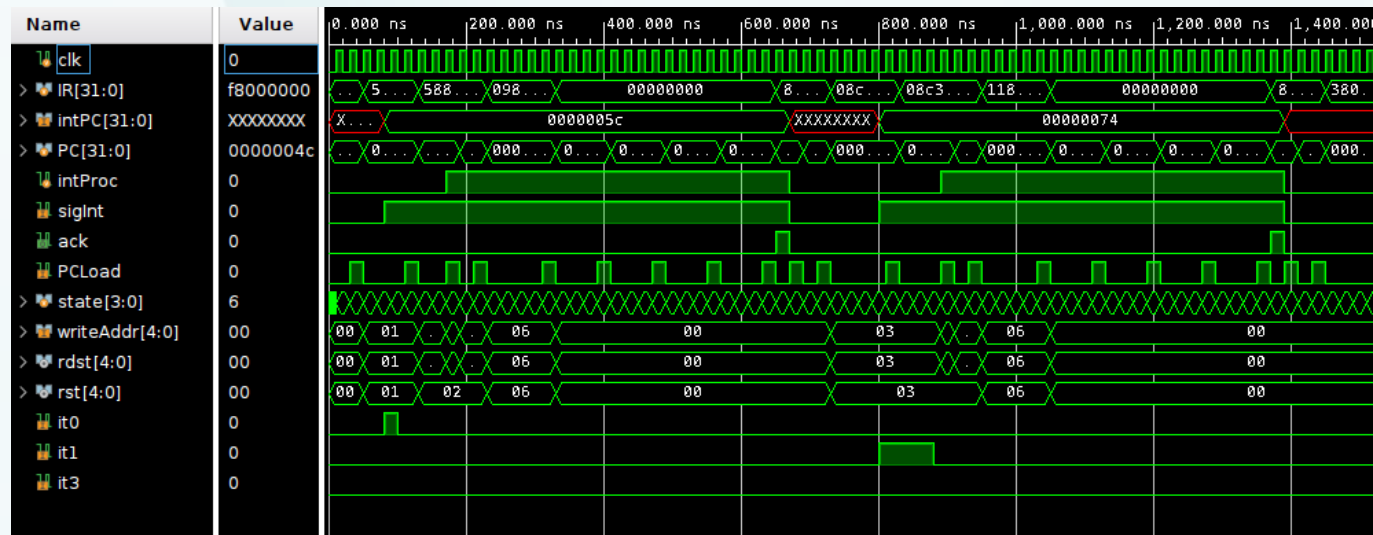

Test Bench DMA

